

Cairo University
Faculty of Computers and Information



CS331

Assignment 2

Computer organization

And architecture

7th Dec 2020

Project Team

Esraa AbuBaker Mubarek 20180040

Marina Moheb Nafee 20180208

Task 2 – Problem Solving

Implement SystemVerilog design for FSM of problem 3.31

[Esraa]

```
module sequenceDetector(q,clk,Reset,x);
output reg q;
input clk,Reset,x;
statetype [1:0] currentstate;
statetype [1:0] nextstate;
typedef enum logic { A=2'b00,B=2'b01,C=2'b10,D=2'b11} statetype;
always@(x,currentstate)
begin
q=(currentstate[0])|(currentstate[1]);
case(currentstate)
A:if(x==0) begin nextstate= B;end
   else begin nextstate= D;end
B:if(x==0) begin nextstate= A;end
   else begin nextstate=C ;end
C:if(x==0|x==1) begin nextstate= B;end
D:if(x==0|x==1) begin nextstate= B;end
endcase
end
always@(posedge clk)
begin
if(~Reset)
currentstate <= nextstate;
else
currentstate =A;
end
endmodule
```

another solution

```
module essr22 (
input reset, input clock, input x,
output y);

enum int unsigned { state1=0, state3=1, state4=2, state2=3 } fstate, reg_fstate;

always_ff @(posedge clock)
begin
if (clock) begin
```

```

        fstate <= reg_fstate;
    end
end

always_comb begin
    if (reset) begin
        reg_fstate <= state1;
        y <= 1'b0;
    end
    else begin
        y <= 1'b0;
        case (fstate)
            state1: begin
                if ((x == 1'b0))
                    reg_fstate <= state2;
                else if ((x == 1'b1))
                    reg_fstate <= state4;
                // Inserting 'else' block to prevent latch inference
                else
                    reg_fstate <= state1;

                if ((x == 1'b1))
                    y <= 1'b1;
                else if ((x == 1'b0))
                    y <= 1'b0;
                // Inserting 'else' block to prevent latch inference
                else
                    y <= 1'b0;
            end
            state3: begin
                reg_fstate <= state2;
            end
            state4: begin
                reg_fstate <= state2;

                y <= 1'b1;
            end
            state2: begin
                if ((x == 1'b1))
                    reg_fstate <= state3;
                else if ((x == 1'b0))
                    reg_fstate <= state1;
            end
        endcase
    end
end


```

```

// Inserting 'else' block to prevent latch inference
else
    reg_fstate <= state2;

if ((x == 1'b1))
    y <= 1'b1;
// Inserting 'else' block to prevent latch inference
else
    y <= 1'b0;
end
default: begin
    y <= 1'bx;
    $display ("Reach undefined state");
end
endcase
end
end
endmodule

```

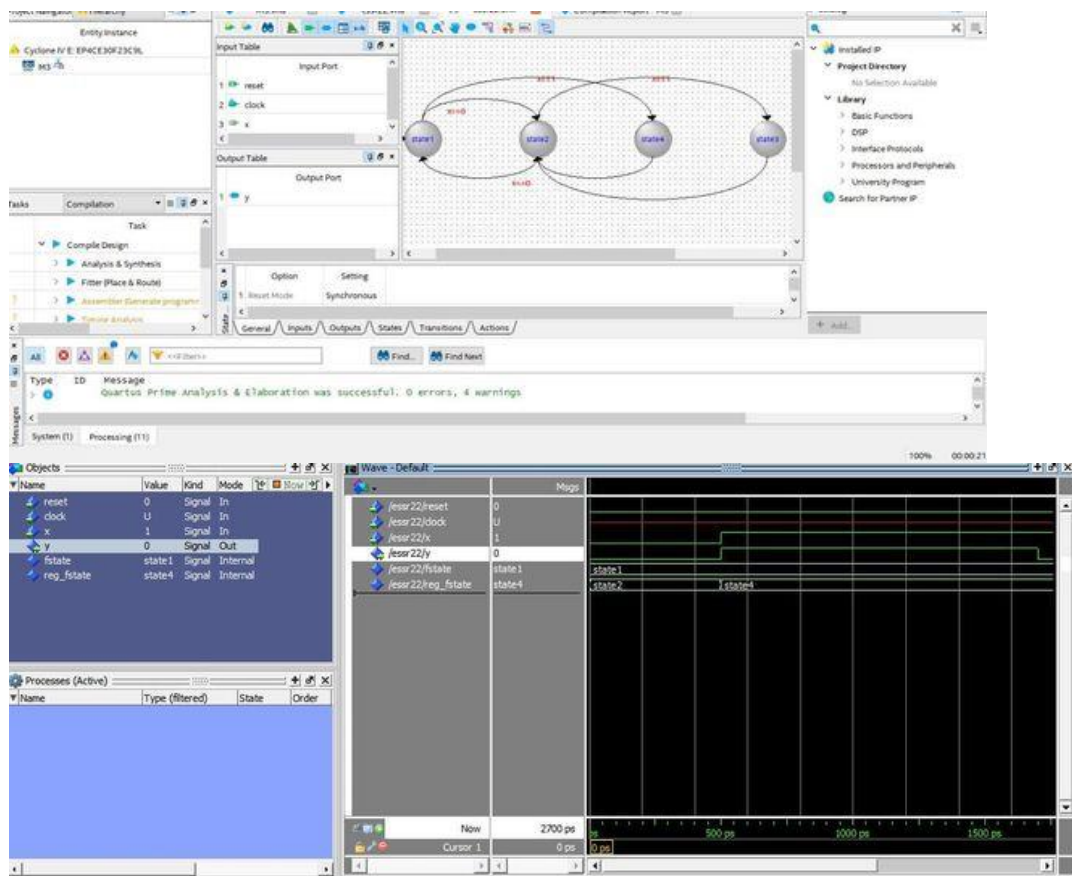

Implement SystemVerilog design for FSM of problem 3.32

[Marina]


```
module SM1 (  
    input reset, input clock, input x,  
    output y);  
  
    enum int unsigned { state1=0, state2=1, state3=2 } fstate, reg_fstate;  
  
    always_ff @(posedge clock)  
    begin  
        if (clock) begin  
            fstate <= reg_fstate;  
        end  
    end  
  
    always_comb begin  
        if (reset) begin  
            reg_fstate <= state1;  
            y <= 1'b0;  
        end  
        else begin  
            y <= 1'b0;  
            case (fstate)  
                state1: begin  
                    if ((x == 1'b0))  
                        reg_fstate <= state1;  
                    else if ((x == 1'b1))  
                        reg_fstate <= state2;  
                    // Inserting 'else' block to prevent latch inference  
                    else  
                        reg_fstate <= state1;  
                end  
                state2: begin  
                    if ((x == 1'b1))  
                        reg_fstate <= state3;  
                    else if ((x == 1'b0))  
                        reg_fstate <= state1;  
                end  
            end  
        end  
    end
```

```

        // Inserting 'else' block to prevent latch inference
        else
            reg_fstate <= state2;
        end
state3: begin
    if ((x == 1'b1))
        reg_fstate <= state3;
    else if ((x == 1'b0))
        reg_fstate <= state1;
    // Inserting 'else' block to prevent latch inference
    else
        reg_fstate <= state3;

    if ((x == 1'b1))
        y <= 1'b1;
    // Inserting 'else' block to prevent latch inference
    else
        y <= 1'b0;
    end
default: begin
    y <= 1'bx;
    $display ("Reach undefined state");
end
endcase
end
end
endmodule

```

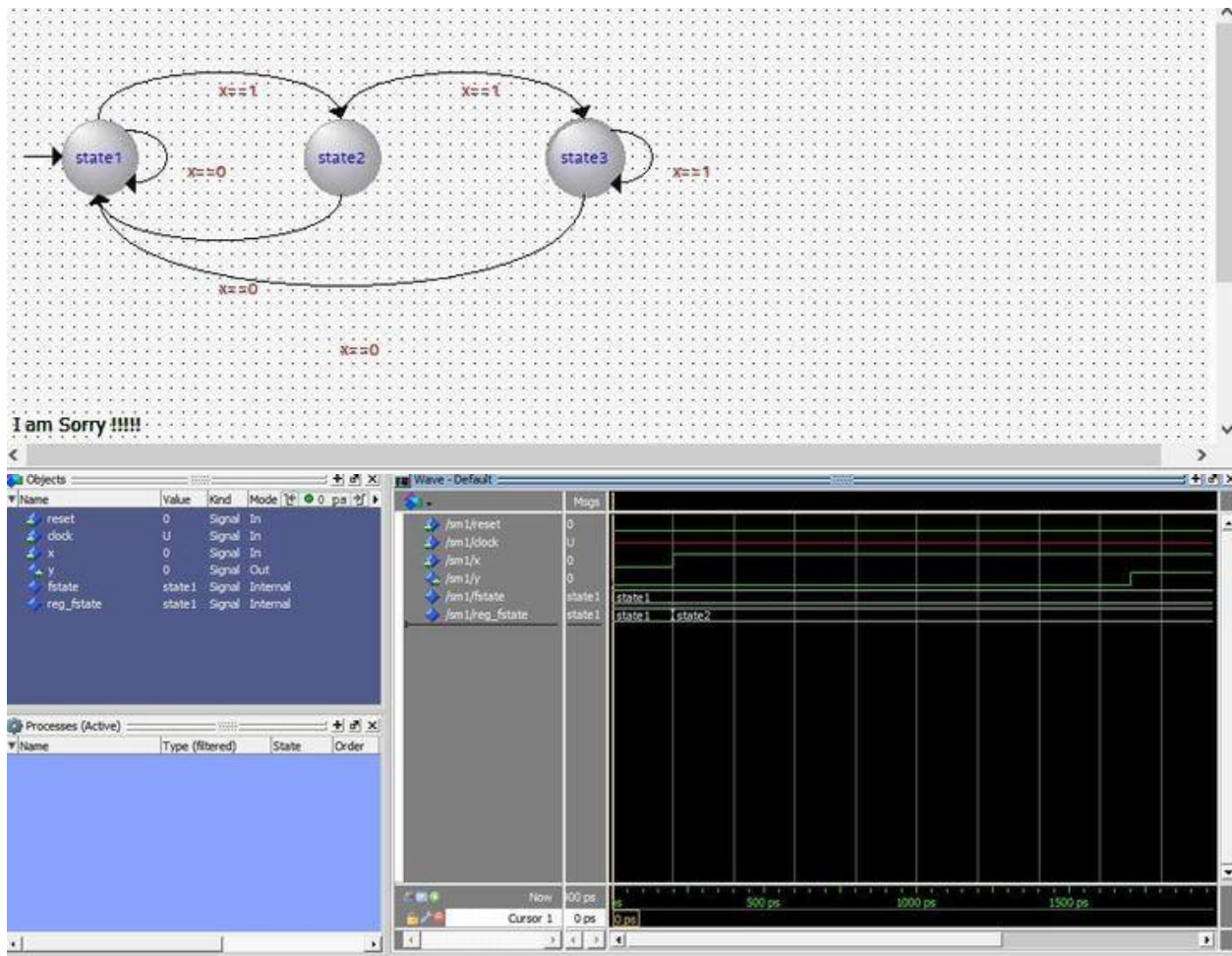

Exercise 4.42

[Esraa]

```
library IEEE; use IEEE.STD_LOGIC_1164.all;
entity ex4_42 is
  port(clk, reset, x: in STD_LOGIC;
        q: out STD_LOGIC);
end;
architecture synth of ex4_42 is type statetype is (S00, S01, S10, S11);
  signal state, nextstate: statetype;
begin
  process(clk, reset) begin
    if reset then state <= S00;
    elsif rising_edge(clk) then
      state <= nextstate;
    end if;
  end process;
  process(all) begin
```

```

case state is
when S00 => if x then
nextstate <= S11;
else nextstate <= S01;
end if;
when S01 => if x then
nextstate <= S10;
else nextstate <= S00;
end if;
when S10 => nextstate <= S01;
when S11 => nextstate <= S01;
when others => nextstate <= S00;
end case;
end process;
q <= '0' when (state = S00) else '1';
end;

```

Exercise 4.44

[Marina]

```

module a(input logic clk, a, b, c, d,
output logic q);
logic reg1, reg2, reg3, reg4;
always_ff @(posedge clk)
begin
reg1 <= a;
reg2 <= b;
reg3 <= c;
reg4 <= d;
q <= ((reg1 ^ reg2) ^ reg3) ^ reg4;
end
endmodule

module d (input logic clk, a, b, c, d,
output logic q);
logic reg1, reg2, reg3, reg4;
always_ff @(posedge clk)
begin
reg1 <= a;
reg2 <= b;
reg3 <= c;
reg4 <= d;
q <= (reg1 ^ reg2) ^ (reg3 ^ reg4);
end
endmodule

```


Exercise 4.46


[Esraa]

Tristate busses can have multiple drivers, so they should be declared as a net.

Exercise 4.48

[Marina]

They have the same function.

 

Exercise 4.50

[Esraa]

Changes are in bold

(a) Error : in always statement d not included

```
module latch(input logic clk,  
             input logic [3:0] d,  
             output reg [3:0] q);  
    always @(clk,d)  
        if (clk) q <= d;  
endmodule
```

(b) Error: in always statement b not included.

```
module gates(input logic [3:0] a, b,  
            output logic [3:0] y1, y2, y3, y4, y5);  
    always @(a,b)  
    begin  
        y1 = a & b;  
        y2 = a | b;  
        y3 = a ^ b;  
        y4 = ~(a & b);  
        y5 = ~(a | b);  
    end
```

```
endmodule
```

- (c) Error : always statement needs to respond to any changes in s not just positive edge

```
module mux2(input logic [3:0] d0, d1,
            input logic s,
            output logic [3:0] y);
    always_comb or always@(d0,d1)
        if (s) y <= d1;
        else y <= d0;
endmodule
```

- (d) Error : in always statement , filpflops have a special always statement , error in the equal sign and begin and end statement .

```
module twoflops(input logic clk,
                input logic d0, d1,
                output logic q0, q1);
    always_ff @(posedge clk)
        begin
            q1 <= d1;
            q0 <= d0;
        end
endmodule
```

- (e) Error: Reset missing in input declaration ,out1 and out2 aren't assigned for all cases and also it would be best to separate the next state logic from the current state.

```
module FSM(input logic clk,
            input logic a,
            input logic Reset,
            output logic out1, out2);
    logic currentstate,nextstate;
    // currentstate logic
    always_ff @(posedge clk,posedge Reset)
        if (Reset)
            currentstate <= 1'b0;
        else
            currentstate <= nextstate;
    // nextstate logic
    always_comb
        case(currentstate)
            1'b0: if (a) nextstate = 1'b1;
            else nextstate = 1'b0;
            1'b1: if (~a) nextstate = 1'b1;
            else nextstate = 1'b0;
        endcase
    // output logic (combinational)
```

```

always_comb
if (currentstate == 0) {out1, out2}={1'b1,1'b0};
else { out1, out2}={1'b0,1'b1};
endmodule

```

Exercise 4.50

[Marina]

(f) **Error:** If must have. Else and it is combinational circuit

```

always_comb
if (a[3]) y = 4'b1000;
else if (a[2]) y = 4'b0100;
else if (a[1]) y = 4'b0010;
else if (a[0]) y = 4'b0001;
else y = 4'b0000;
endmodule

```

(g) **Error:** state S2 is missing and default is missing

```

module divideby3FSM(input logic clk,
                    input logic reset,
                    output logic out);
    logic [1:0] state, nextstate;
    parameter S0 = 2'b00;
    parameter S1 = 2'b01;
    parameter S2 = 2'b10;
    // State Register
    always_ff @(posedge clk, posedge reset)
        if (reset) state <= S0;
        else state <= nextstate;
    // Next State Logic
    always_comb
        case (state)
            S0: nextstate = S1;
            S1: nextstate = S2;
            S2: nextstate = S0;
            default: nextstate = S0;
        endcase
    // Output Logic
    assign out = (state == S2);
endmodule

```

(h) **Error:** two statement have the same value so ~ is missing on the first tristate.

```

module mux2tri(input logic [3:0] d0, d1,
               input logic s,
               output logic [3:0] y);
    tristate t0(d0, ~s, y);
    tristate t1(d1, s, y);
endmodule

```

(i) **Error:** q, cannot be assigned in multiple always or assignment statements.

```
module floprs(input logic clk,
              input logic reset,
              input logic set,
              input logic [3:0] d,
              output logic [3:0] q);
always_ff @(posedge clk, posedge reset, posedge set)
  if (reset) q <= 0;
  else if (set) q <= 1;
  else q <= d;
endmodule
```

(j) **Error:** combinational module so statements (=) should be used in the always statement.

```
module and3(input logic a, b, c,
            output logic y);
  logic tmp;
  always_comb
  begin
    tmp = a & b;
    y = tmp & c;
  end
endmodule
```

Task 3 – FP Multiplier

```
module add #(parameter x=8)(input logic [x-1:0] exp1,exp2,output logic[x-1:0] y);
  assign y=exp1+exp2-127;
endmodule
```

```
module mult #(parameter x=23)(input logic [x-1:0] mant1,mant2,output logic[47:0] y);
  logic[x:0]m1,m2;
  assign ma={1'b1,mant1};
  assign mb={1'b1,mant1};
  assign y = mant1 * mant2;
endmodule
```

```
module sign #(parameter x=1)(input logic sign1,sign2,output logic m);
  assign m=sign1 ^ sign2;
endmodule
```

```

module norm #(parameter x=8)(input logic [47:0] result,input logic[x-1:0] expo,output logic[22:0]
y,output logic[x-1:0]expres);
assign y = result[47] ?result[46:24] :result[45:23];
assign expres=expo-1;
endmodule

```

```

module fp(input logic [31:0] a, b,output logic [31:0] m);
logic [7:0] expa, expb, expres,expo;
logic [23:0] manta, mantb,mantres;
logic signa,signb,signres;
logic [47:0] result;
assign {expa, manta} = {a[30:23], a[22:0]};
assign {expb, mantb} = {b[30:23], b[22:0]};
assign signa=a[31];
assign signb=b[31];
mult(manta,mantb,result);
add(expa,expb,expo);
sign(signa,signb,signres);
norm(result,expo,mantres,expres);
assign m={signres,expres,mantres};
endmodule

```

```


module test1 ();
logic [31:0] a,b,y;
fp(a,b,y);
intial begin
    a=32'b01100000000000000000000000000000;
    b=32'b11001000000000000000000000000000;
    if(y==32'b00000100110000000000000000000000) $display("right answer");
end
endmodule

```

```

module test ();
logic [31:0] a,b,y;
fp(a,b,y);
intial begin
    a=32'b00111111100001100110011001100110;
    b=32'b00111111100001100110011001100110;
    if(y==32'b001111111000011010001111010110111) $display("right answer");
end
endmodule

```

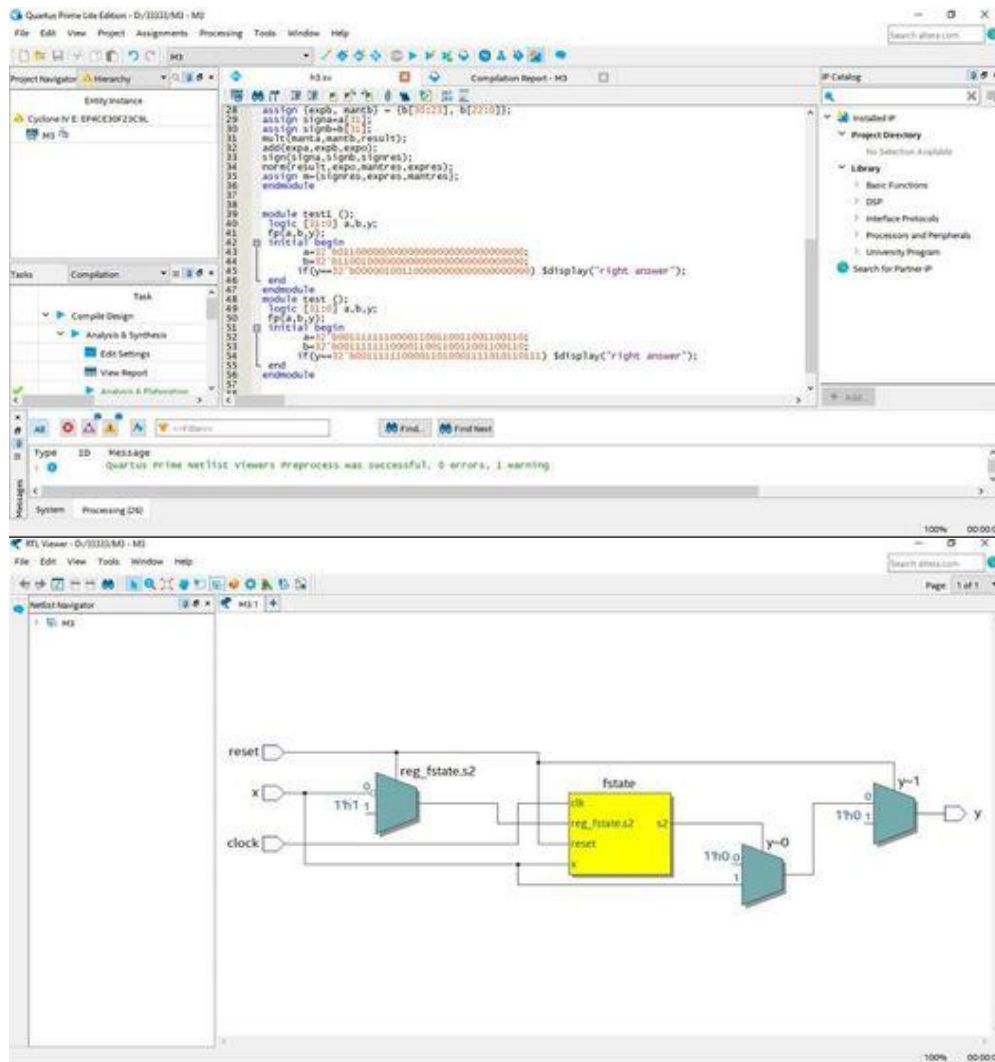

Task 4 – ALU

Exercise 5.9

```

module ALU32(input logic [31:0] A, B,
             input logic [2:0] F,
             output logic [31:0] Y);



    logic [31:0] S, BB;
    assign BB = F[2] ? ~B : B;
    assign S = A + BB + F[2];
    always_comb

```

```

begin
  case (F[1:0])
    2'b00: Y <= A & BB;
    2'b01: Y <= A | BB;
    2'b10: Y <= S;
    2'b11: Y <= S[31];
  endcase
end
endmodule

```

  

Exercise 5.10

(b)




(C) module ALUwithOverflow(input logic [31:0] A, B,
 input logic [2:0] F,
 output logic Overflow,

```

                                output logic [31:0] Y);
logic [31:0] S, BB;
assign BB = F[2] ? ~B : B;
assign S = A + BB + F[2];
always_comb
begin
    case (F[1:0])
        2'b00: Y <= A & BB;
        2'b01: Y <= A | BB;
        2'b10: Y <= S;
        2'b11: Y <= S[31];
    endcase
end
    always_comb
    case (F[2])
        1'b0: Overflow = A[31] & B[31] & ~S[31] |
                    ~A[31] & ~B[31] & S[31];
        1'b1: Overflow = ~A[31] & B[31] & S[31] |
                    A[31] & ~B[31] & ~S[31];
        default: Overflow = 1'b0;
    endcase
endmodule

```

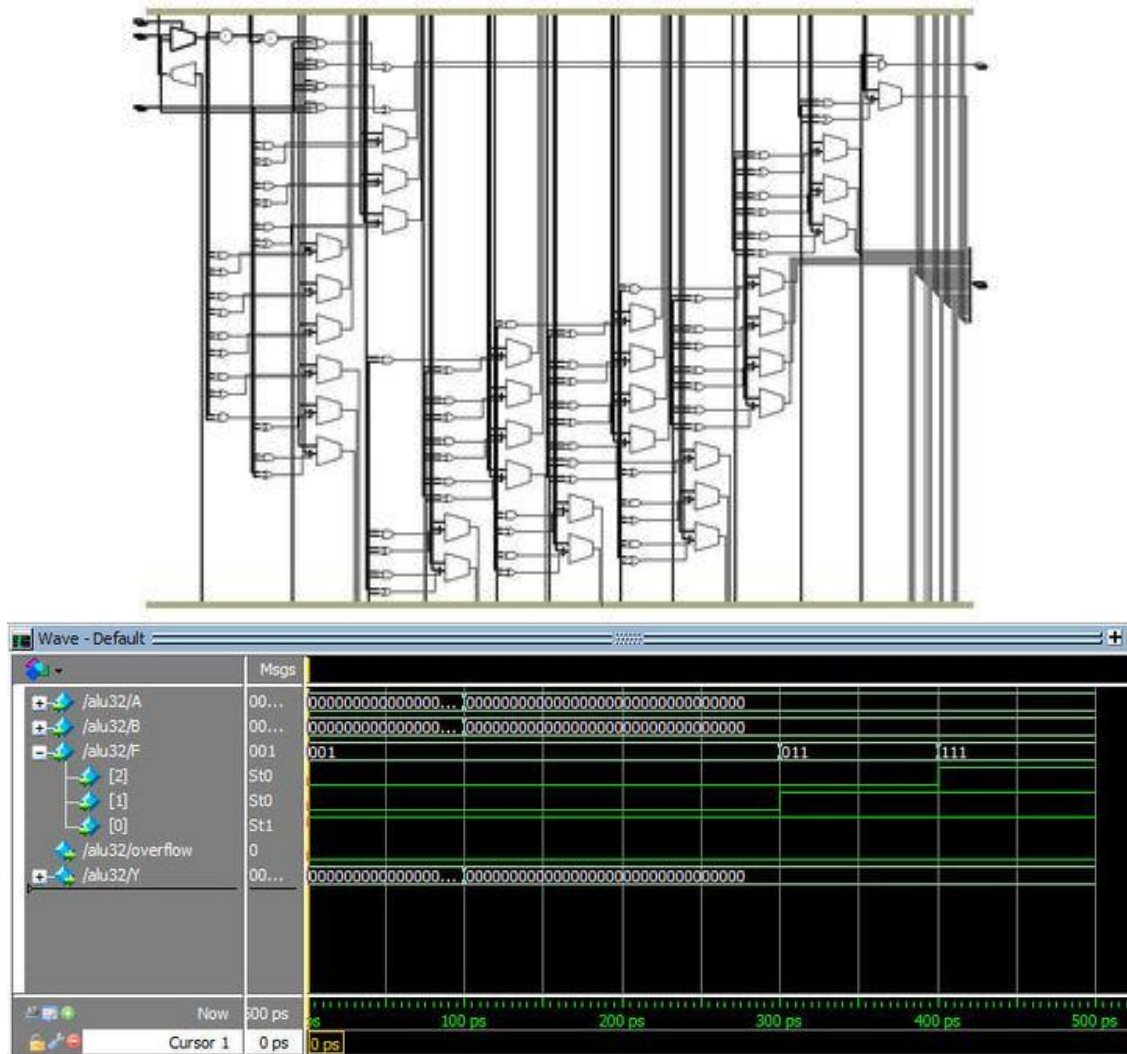Exercise 5.11

```

module ALUwithZero(input logic [31:0] A, B,
                  input logic [2:0] F,
                  output logic Overflow,
                  output logic zero,
                  output logic [31:0] Y);

    logic [31:0] S, BB;
    assign BB = F[2] ? ~B : B;
    assign S = A + BB + F[2];
always_comb
    begin
        case (F[1:0])
            2'b00: Y <= A & BB;

```

```

        2'b01: Y <= A | BB;
        2'b10: Y <= S;
        2'b11: Y <= S[31];
    endcase
end
assign zero = (Y==0);
always_comb
    case (F[2:1])
        2'b01: Overflow = A[31] & B[31] & ~S[31] |
                        ~A[31] & ~B[31] & S[31];
        2'b11: Overflow = ~A[31] & B[31] & S[31] |
                        A[31] & ~B[31] & ~S[31];
        default: Overflow = 1'b0;
    endcase
endmodule

```

